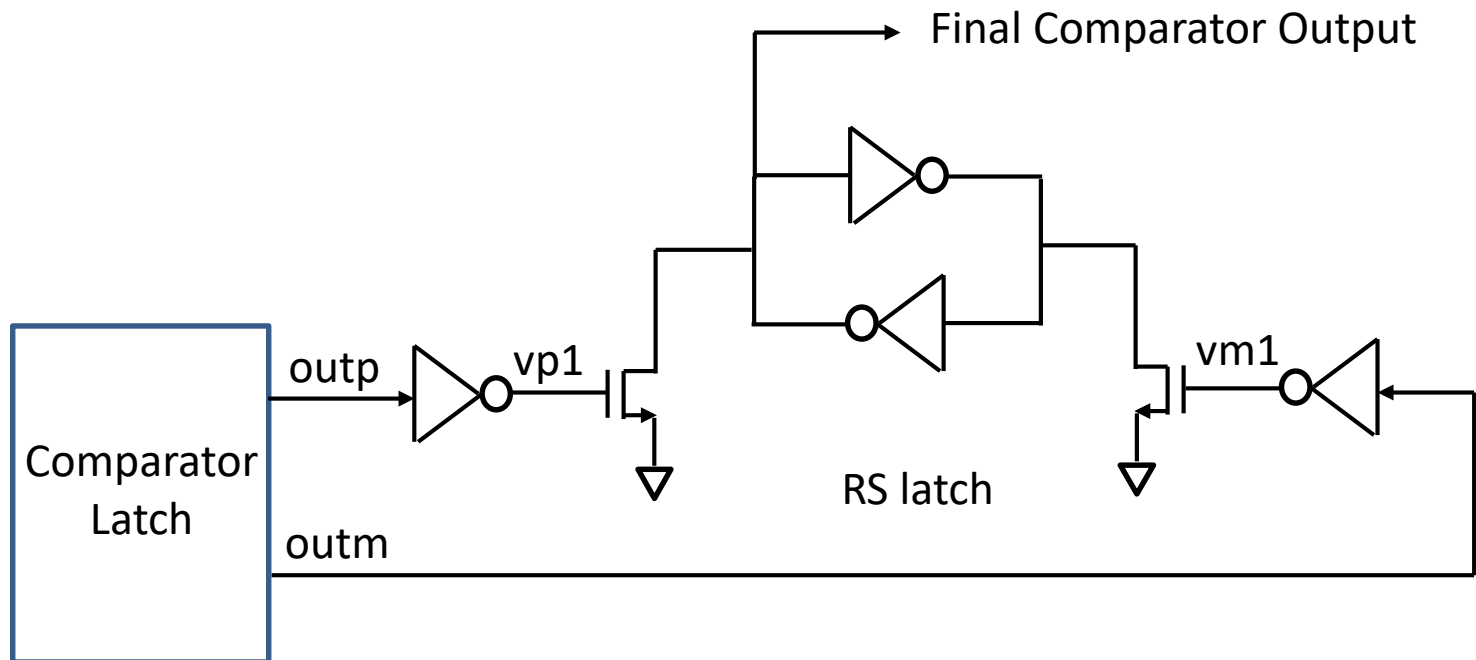


# HW4 Comparator RS latch implementation



During ph2, comparator latch makes a decision.

During ph1, both comparator latch outputs (outp, outm) reset to VDD.

Then both vp1 & vm1 are low, thereby retaining previous outputs.