
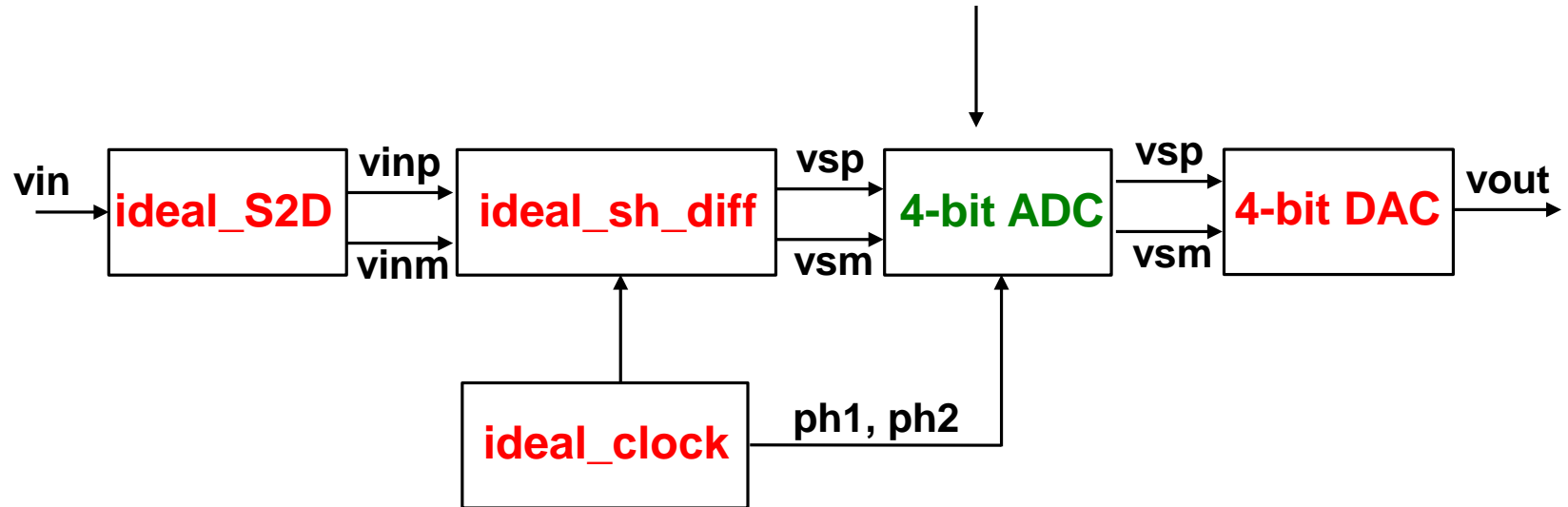


EE288 HW#4 : 4-bit Flash ADC

Real comparators using nmos2v and pmos2v

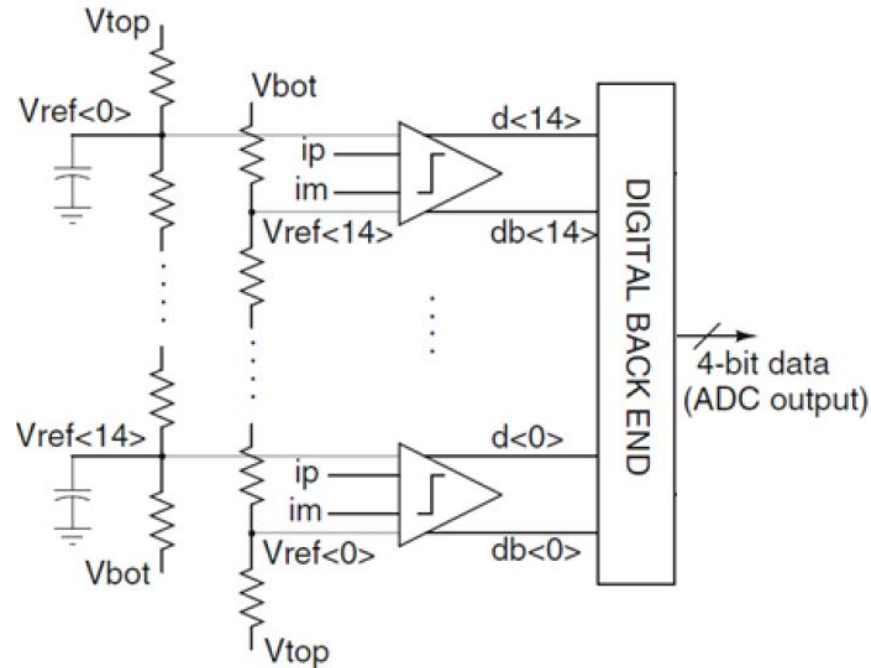

HW#4 : 4-bit Flash ADC




- Your goal is to minimize the ADC Figure of Merit given by $FoM = \text{Power} / (f_s \cdot 2^{ENOB})$.
- Use `ideal_swn`, `ideal_swp`, `ideal_clock`, `ideal_S2D`, `ideal_sh_diff` from `ee288lib`

HW4 Simulation Test Bench – See EE288HW4 in ee288lib

You are designing 4-bit Flash ADC in HW4.

EE288HW4 in ee288lib

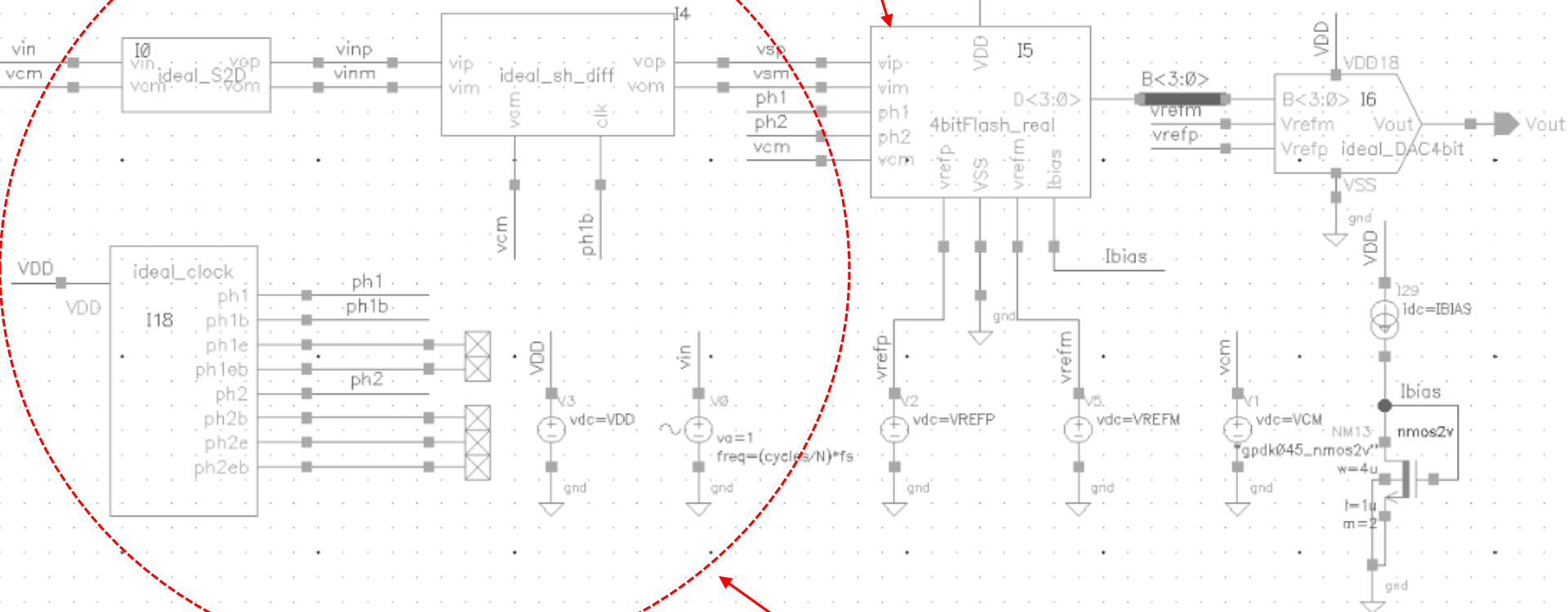


Copy these blocks to set up the simulation environment.

Comparator Test

- Key block in Flash ADC is Comparator.
- There are several options for comparator architectures.
- You will need a preamp + latch structure.
- The following slides show some options for preamps and latches.
- The output of the latch will be followed by a RS latch.
- Comparator overdrive test should show the output sequence 1011.
- See Comparator overdrive test bench in “comparator_tb” in ee288lib


Comparator Overdrive Test Bench

comparator_tb in ee288lib

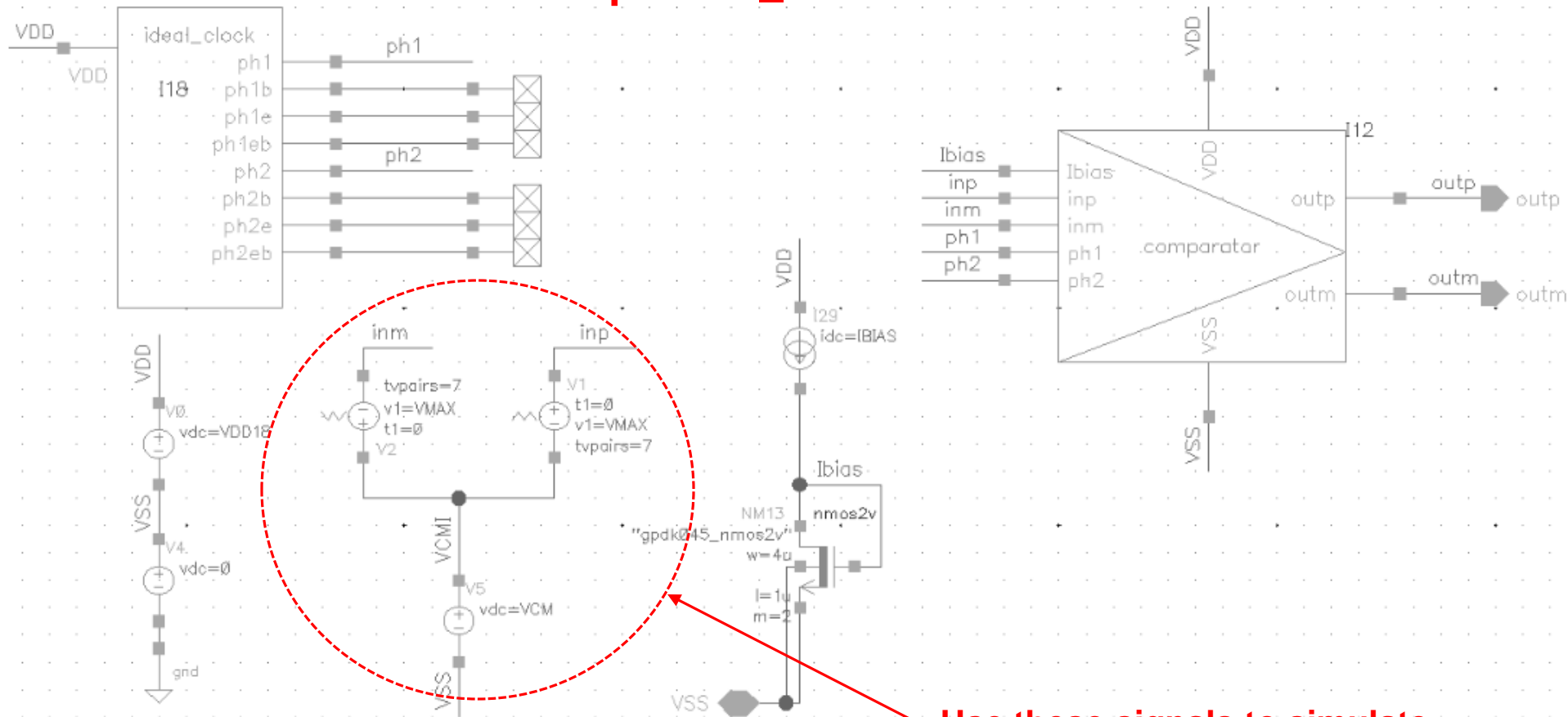


**Use these signals to simulate
The comparator overdrive test.
VMAX=0.4, VMIN=10mV**


Comparator Architecture Option 1

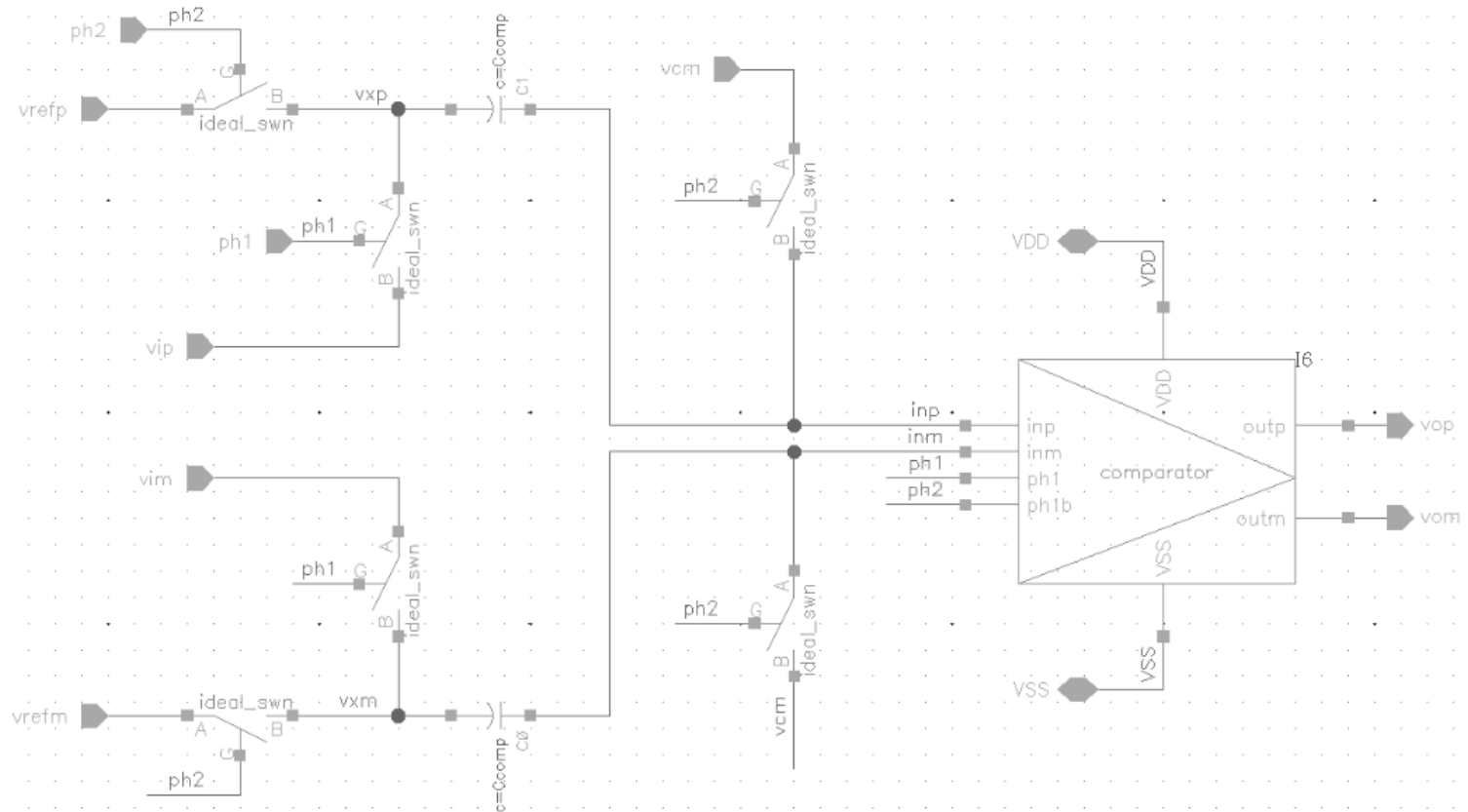


Comparator Architecture Option 2

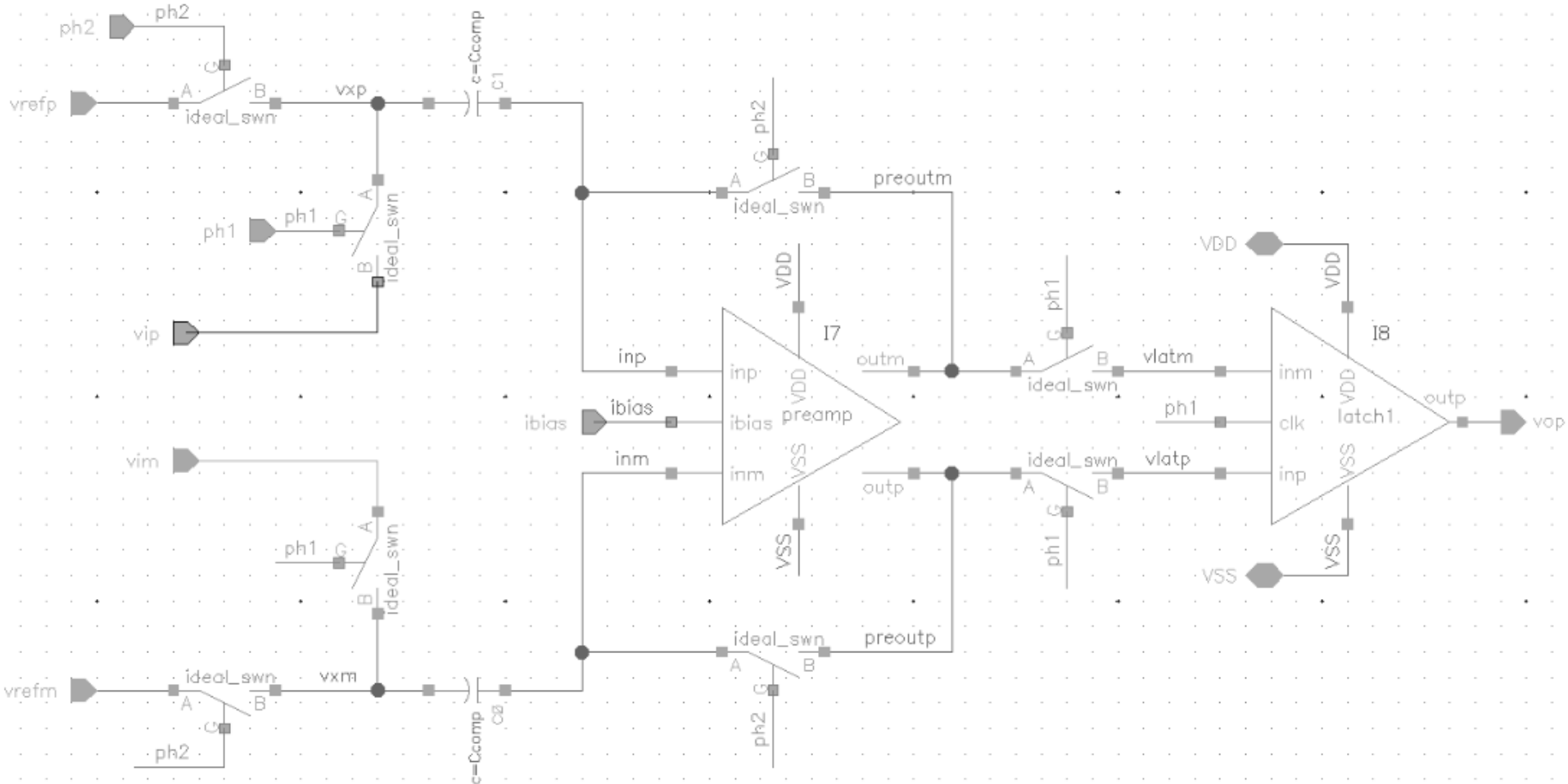


Differential Amplifier Example 1

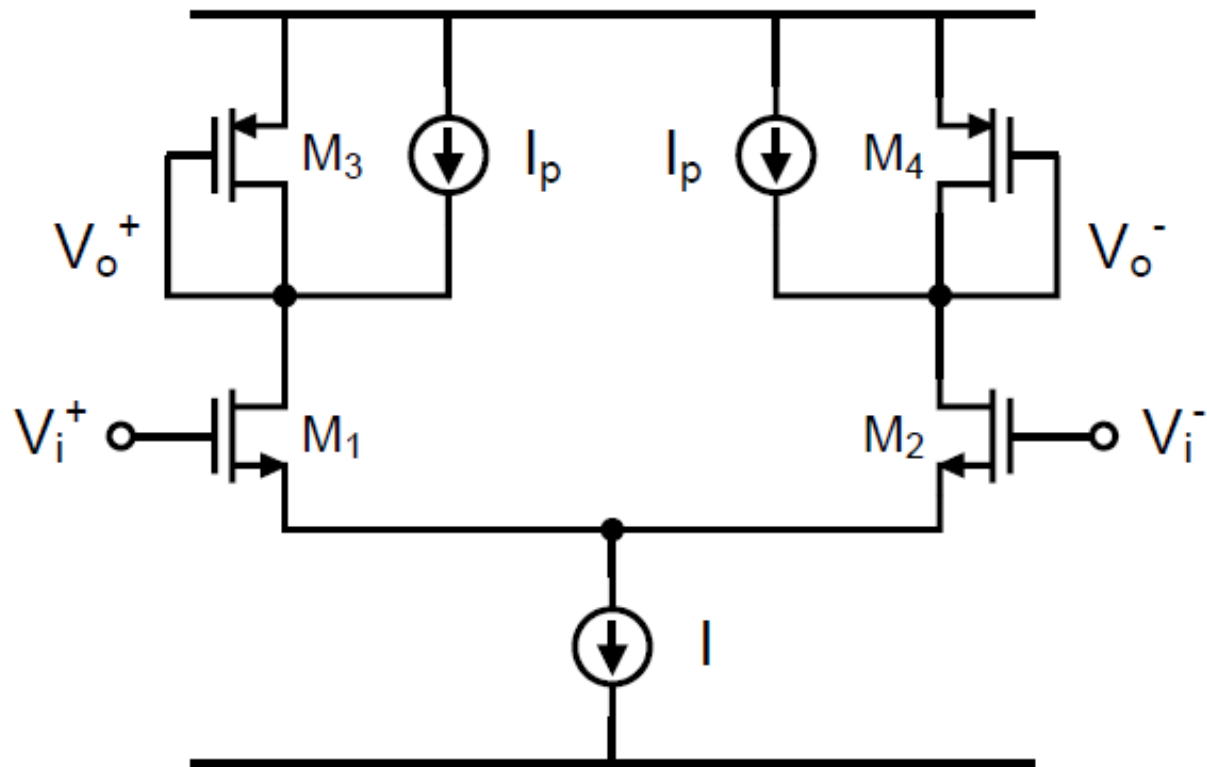


Differential Amplifier Example 2

 


Differential Amplifier Example 3

 


Latched Comparator Example 1

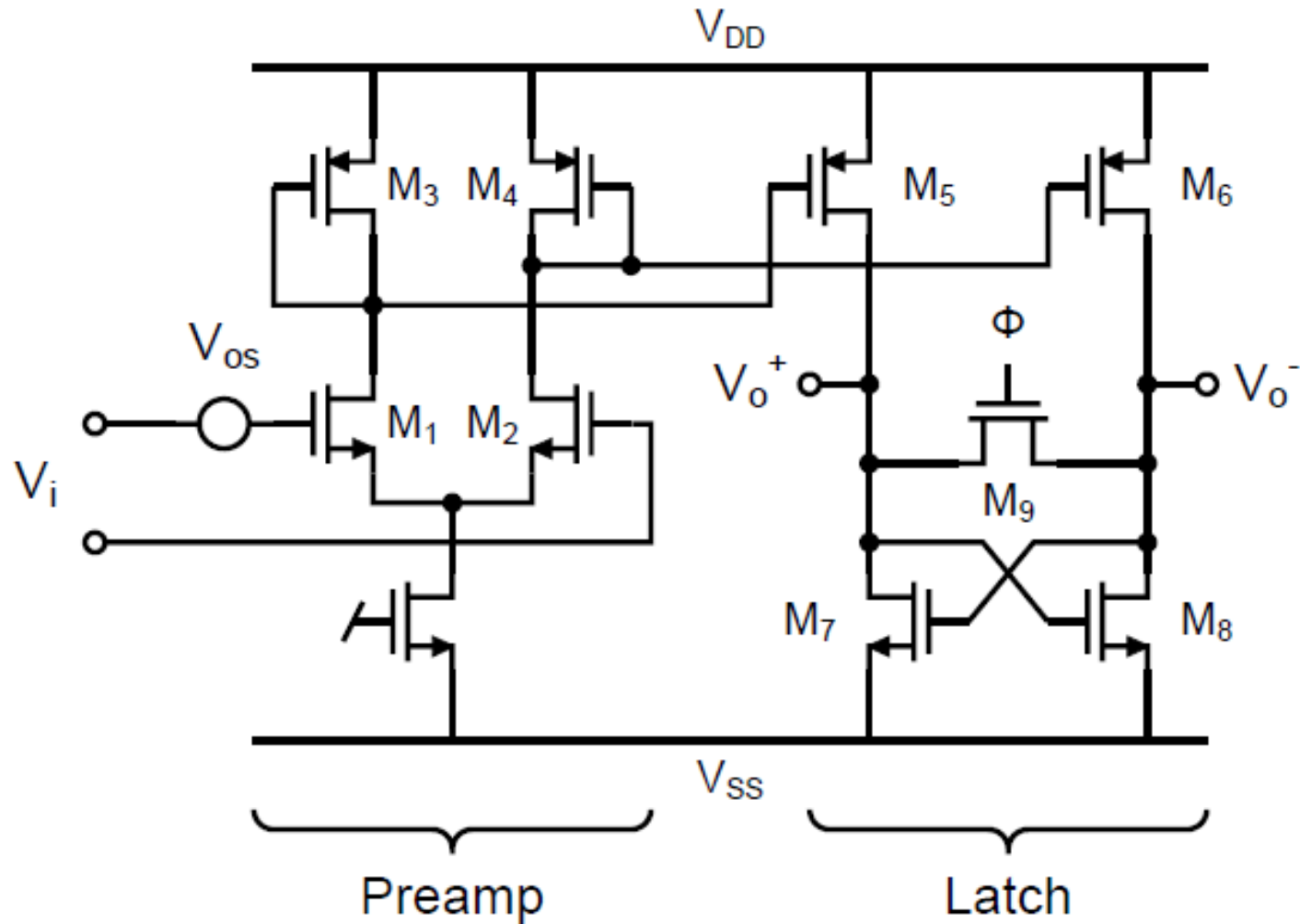

Latch Example 2

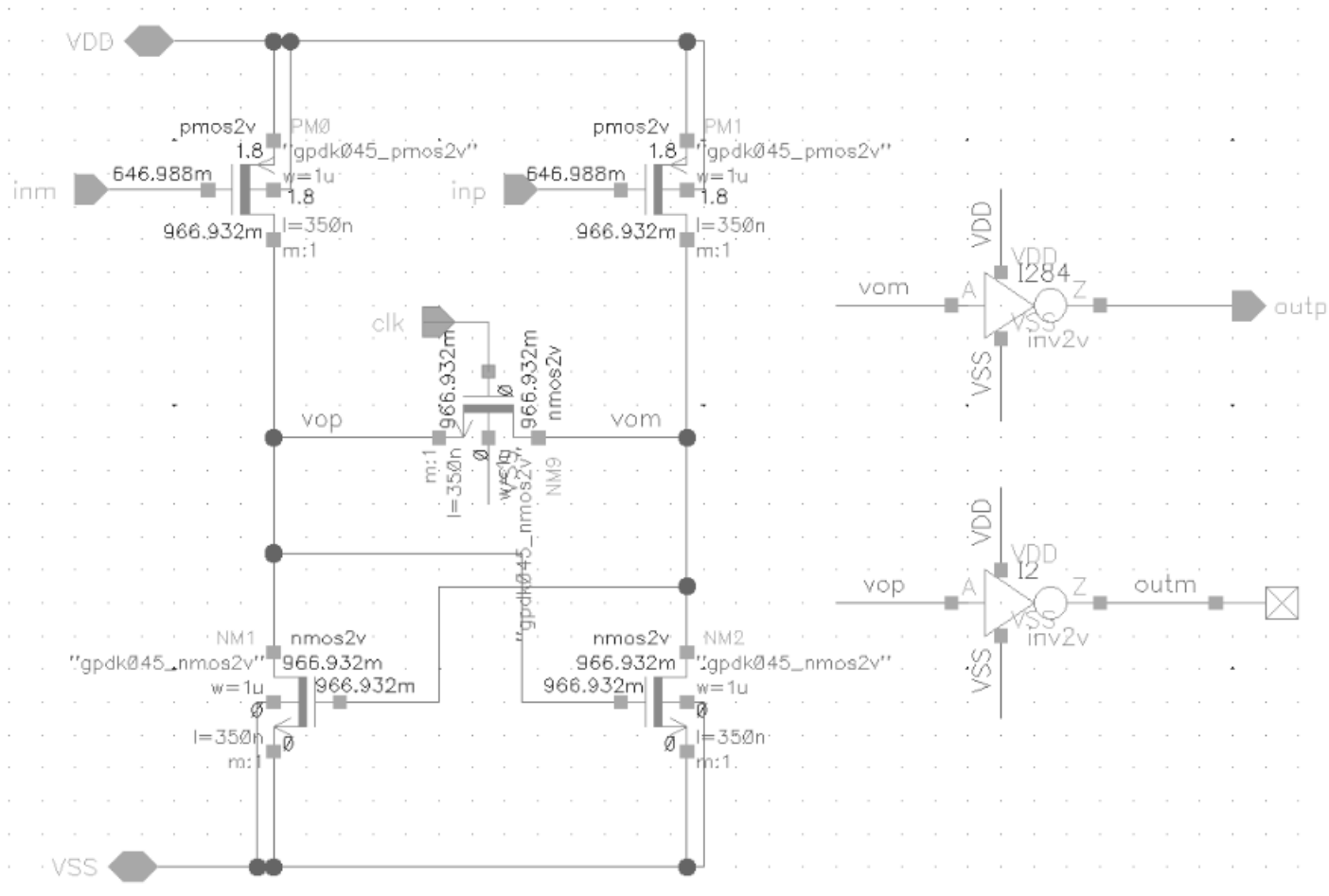

RS latch


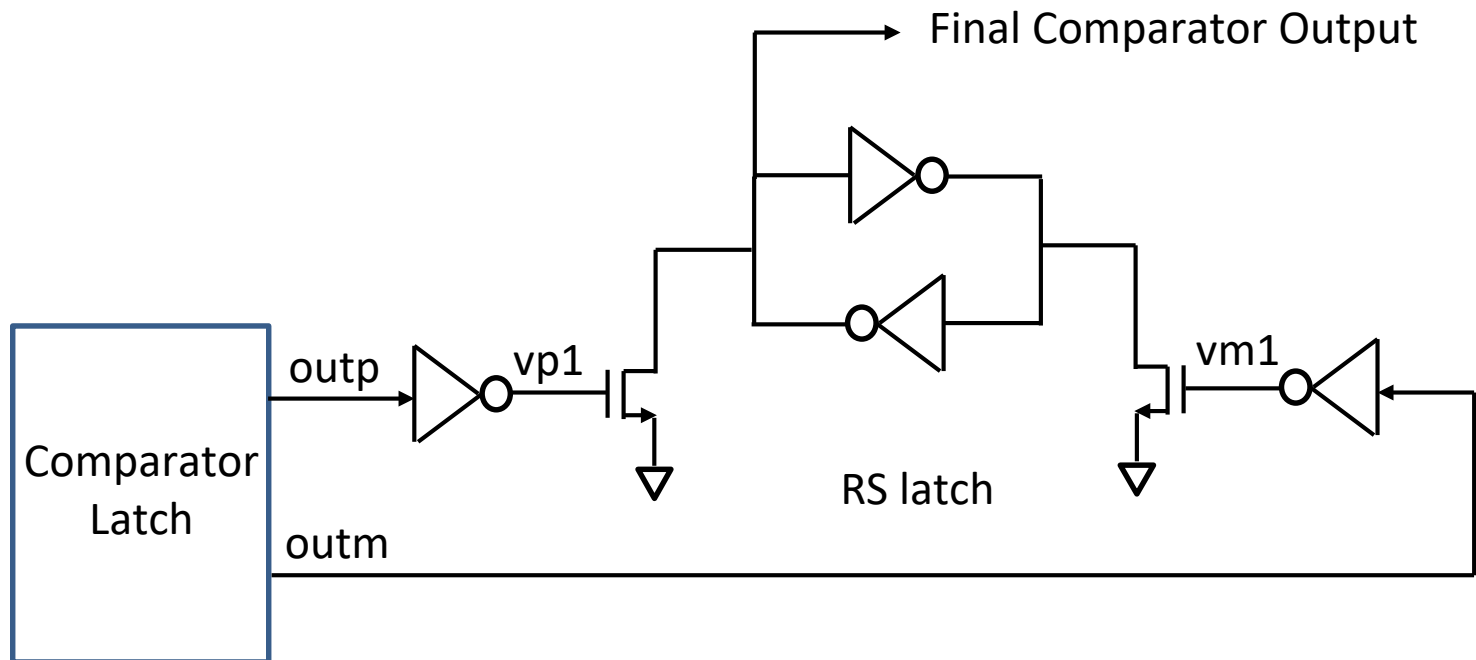


During ph2, comparator latch makes a decision.


During ph1, both comparator latch outputs (outp, outm) reset to VDD.

Then both vp1 & vm1 are low, thereby retaining previous outputs.

HW#4 : Comparator Overdrive Test Bench

  

Comparator Overdrive Test Result

 

4-bit Flash ADC Simulation Result

